


Digital systems and basics of electronics - SYC

10 Sequential Circuits - introduction


Flip-flops and “memory effect”

- **Flip-Flops and Digital Memory:** Flip-flops are fundamental building blocks in digital electronics, used **to store a single bit of data**. They play a key role in creating memory circuits.
- **Memory Effect:** Flip-flops exhibit a "memory effect," meaning they retain their state (0 or 1) until explicitly changed by an input signal, making them ideal for sequential logic and state retention.
- **Types and Applications:** Common types include **SR, D, JK, and T flip-flops**, each designed for specific use cases like counters, data storage, and synchronization in digital systems.


RS Flip-Flop NAND

 

RS Flip-Flop NAND

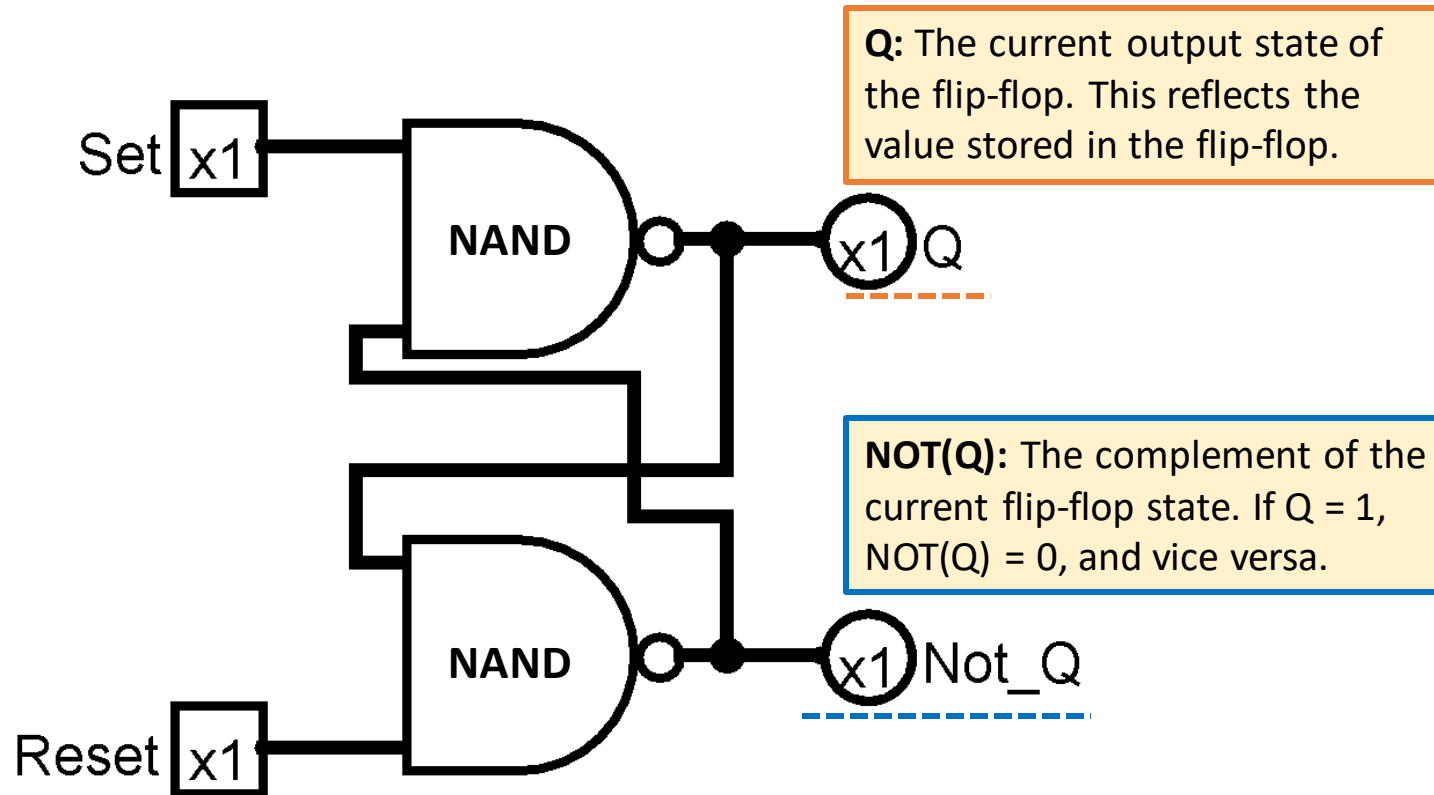

RS Flip-Flop NAND

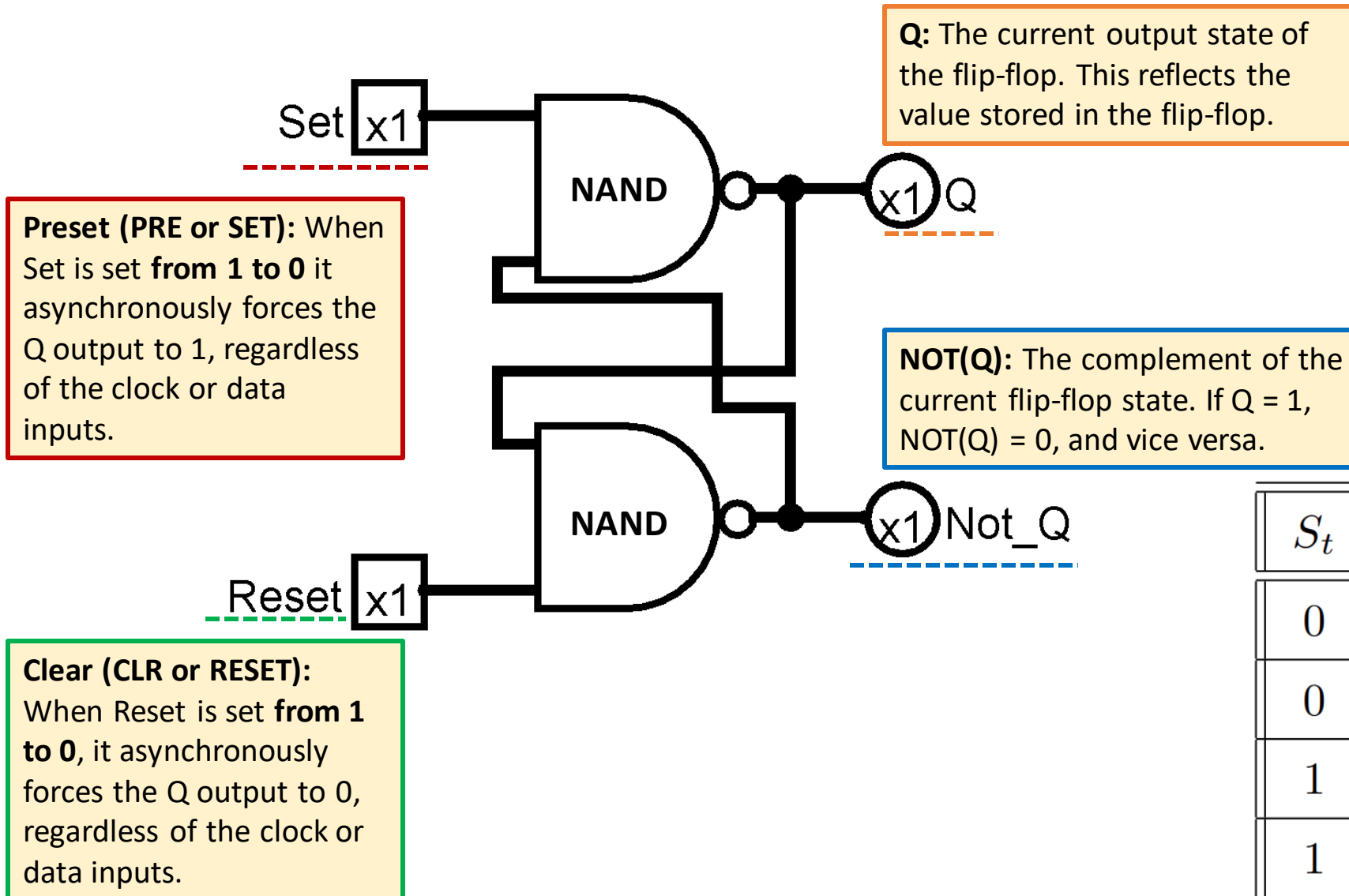


S_t	R_t	Q_{t+1}
0	0	<i>forbidden</i>
0	1	1
1	0	0
1	1	Q_t (previously)

Start logisim

Icon




Version

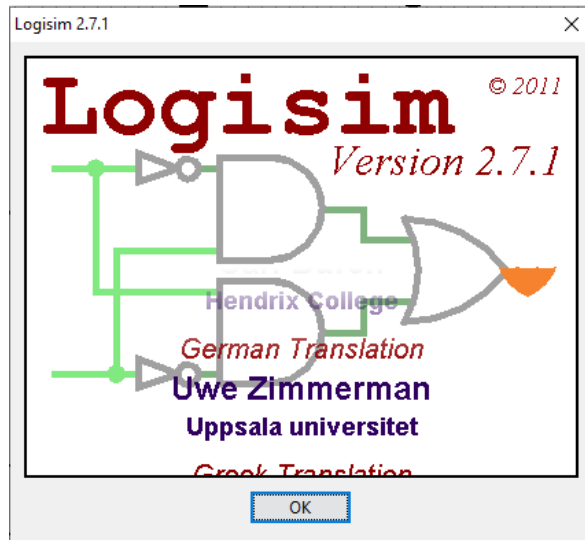


Open :

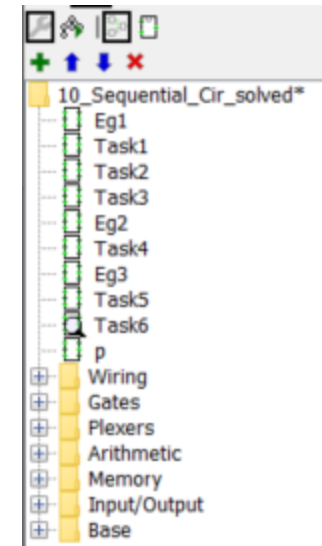[mmajew/SYC/10/10_template_Seq.circ](#)
→ eg1




D Flip-flop

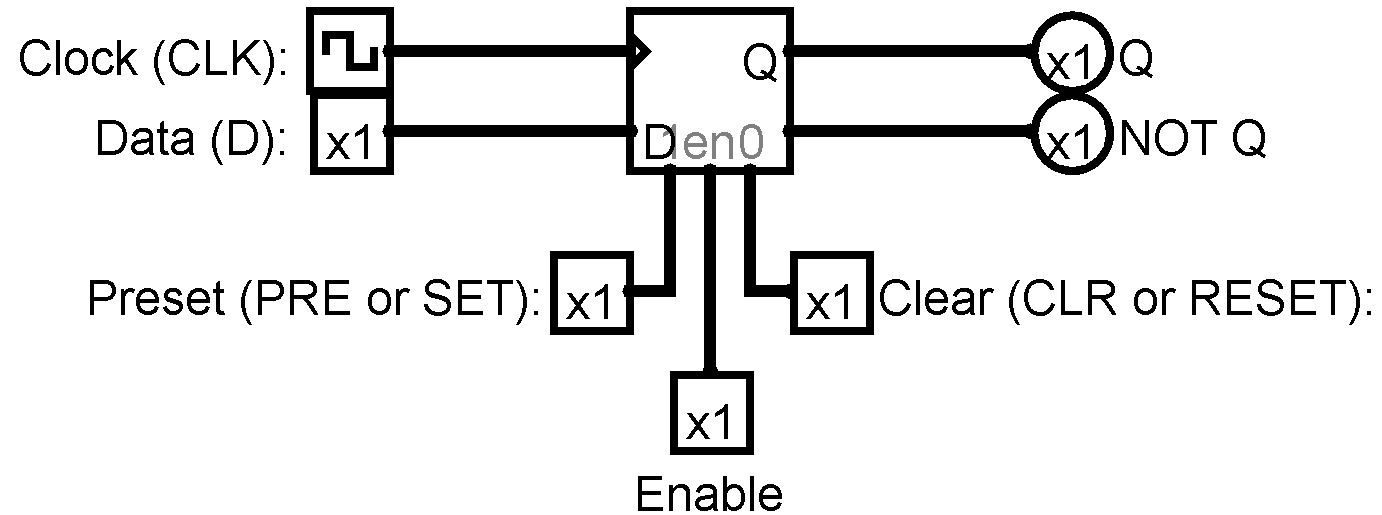

D Flip-flop

Clock (CLK): The flip-flop updates its state on the rising (from 0 to 1) edge of the clock signal, depending on the design. The clock is the primary control signal for synchronous operation.

 Q: The current output state of the flip-flop. This reflects the value stored in the flip-flop.




D Flip-flop

Clock (CLK): The flip-flop updates its state on the rising (from 0 to 1) edge of the clock signal, depending on the design. The clock is the primary control signal for synchronous operation.

Q: The current output state of the flip-flop. This reflects the value stored in the flip-flop.

Data (D): This is the input data pin. The state of this pin (0 or 1) is sampled and stored in the flip-flop on the triggering edge of the clock.

 NOT(Q): The complement of the current flip-flop state. If $Q = 1$, $\text{NOT}(Q) = 0$, and vice versa.




D Flip-flop

Clock (CLK): The flip-flop updates its state on the rising (from 0 to 1) edge of the clock signal, depending on the design. The clock is the primary control signal for synchronous operation.

Q: The current output state of the flip-flop. This reflects the value stored in the flip-flop.

 Data (D): This is the input data pin. The state of this pin (0 or 1) is sampled and stored in the flip-flop on the triggering edge of the clock.



NOT(Q): The complement of the current flip-flop state. If $Q = 1$, $\text{NOT}(Q) = 0$, and vice versa.

Preset (PRE or SET):
When this input is set to 1 (active), it asynchronously forces the Q output to 1, regardless of the clock or data inputs.

Enable (EN): When this input is 0, the clock is ignored, and the flip-flop does not respond to clock edges. When $\text{EN} = 1$, the flip-flop operates normally, responding to the clock.

Clear (CLR or RESET):
When this input is set to 1 (active), it asynchronously forces the Q output to 0, regardless of the clock or data inputs.

Tasks description

- 1. 4-Bit Shift Register:** Using D-type flip-flops, design a 4-bit shift register with the following sequence: 0000 → 1000 → 1100 → 1110 → 1111
1 point
- 2. Ring Counter:** Build a ring counter using the shift register from Task 1. The bits should circulate through the connected stages in a circular fashion
0.5 point
- 3. Johnson Counter:** Design a Johnson counter (also known as a twisted ring counter) using the shift register from Task 1. The counter should follow the sequence: 0000 → 0001 → 0011 → 0111 → 1111 → 1110 → 1100 → 1000 → 0000
0.5 point
- 4. Pseudo-Random Binary Sequence (PRBS) Generator:** Create a PRBS generator by using the shift register from Task 1 along with an XOR logic gate. Ensure the sequence generated is a maximal-length pseudo-random binary sequence.
0.5 point
- 5. Mod-9 Counter:** Using D-type flip-flops, design a counter that cycles through a modulus of 9, with states ranging from `0000` to `1000`.
0.5 point
- 6. Custom Counter (X to Y):** Using D-type flip-flops, build a counter that starts at `X` and ends at `Y`, cycling through the sequence. The values of X and Y are assigned to each student according to the scheme on the next slide.
2 point

Task 6. Custom Counter (X to Y)

The values of X and Y in task 6 are assigned according to your place in the classroom.

The diagram shows a 4x2 grid of cells. Each cell is represented by a blue rectangle with a black border. Below each rectangle, the values of X and Y are listed. The values are as follows:


Row	Column	X	Y
1	1	0001	1110
1	2	0001	1101
2	1	0010	1110
2	2	0010	1101
3	1	0101	1110
3	2	0101	1101
4	1	0100	1110
4	2	0100	1101

Start logisim

Icon



Version

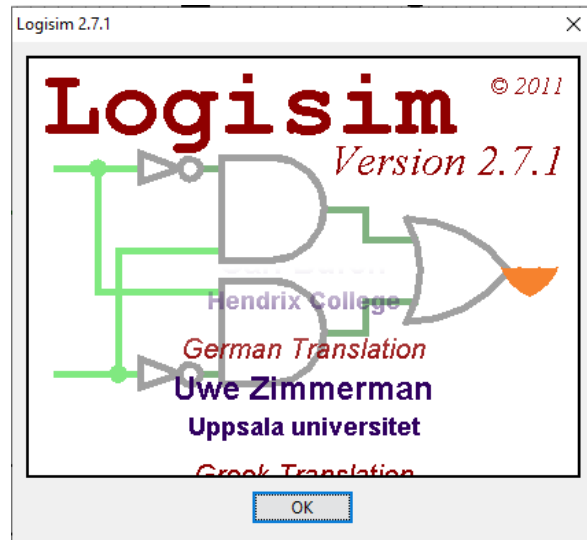

Open :

[mmajew/SYC/10/10_template_Seq.circ](#)

→ task_1


→ task_2

→ task_3


→ task_4

→ task_5


→ task_6

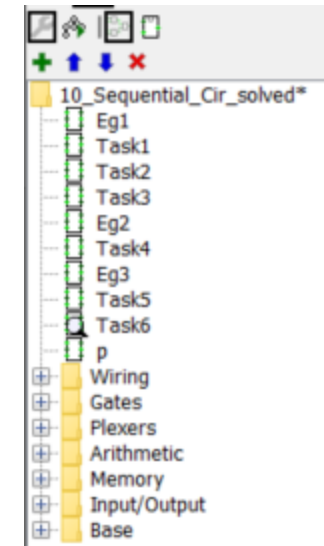

 
Task 1 Using D-type flip-flops build 4-bit shift register: 0000,1000,1100,1110,1111.



 
Task 2 Using shift register from point 1. build ring counter:
the bits circulate through the connected stages in a circular fashion.



 
Task 3 Using shift register from point 1. build Johnson counter:
0000,0001,0011,0111,1111,1110,1100,1000,0000



 Task 4 Using shift register from point 1. and XOR logic gate make PRBS
Pseudo Random Binary Signal generator



 Task 5 Using D-type flip-flops build mod9 counter (from 0000 to 1000)



Task 6 Using D-type flip-flops build counter from 0011 to 1000

